



**DIPLOMA IN ELECTRONICS AND COMMUNICATION ENGINEERING**

**CENTRALIZED QUESTION BANK**

**1040234440- MEASURING INSTRUMENTS AND SENSORS**

**DIRECTORATE OF TECHNICAL  
EDUCATION GOVERNMENT OF  
TAMILNADU**

## DIPLOMA END SEMESTER / YEAR EXAMINATION – 2025

**Course:** Electronics and Communication Engineering

**Subject :** Measuring Instruments and sensors

**QP Code :**1040234440

**Time :** 3 Hours

**Date :**

**Session:**

**Max Marks:**100

### Answer the following Questions

- 1 Extend the range of the given voltmeter.
- 2 Extend the range of the given ammeter.
- 3 Show how the range of the given voltmeter can be extended.
- 4 Show how the range of the given ammeter can be extended.
- 5 Compute the value of multiplier resistances for different range extension of the given voltmeter.
- 6 Compute the value of shunt resistances for different range extension of the given ammeter.
- 7 Calibrate the given ammeter
- 8 Calibrate the given voltmeter.
- 9 Determine the unknown resistance using the Wheatstone bridge.
- 10 Construct a bridge circuit for the measurement of unknown resistance.
- 11 Measure the value of unknown resistance using a bridge circuit.
- 12 Determine the self-inductance of an unknown coil using Maxwells bridge.
- 13 Construct a bridge circuit for the measurement of self-inductance of a coil.
- 14 Measure the value of self-inductance of a coil by using a bridge circuit.
- 15 Determine the capacitance of an unknown capacitor using Schering bridge.
- 16 Measure the value of unknown capacitance using a bridge circuit.
- 17 Construct a bridge circuit for the measurement of unknown capacitance.
- 18 Measurement of voltage, frequency, time period and phase of any periodic waveform using CRO.
- 19 Using CRO, show how amplitude, frequency, time period and phase can be measured in a periodic waveform.
- 20 Carry out amplitude, time period and phase measurement using CRO for
- 21 sinusoidal waveform.
- 22 Measurement of voltage, frequency time period and phase of any periodic waveform using DSO.
- 23 Using DSO, show how amplitude, frequency, time period and phase can be measured in a periodic waveform.
- 24 Carry out amplitude, time period and phase measurement using DSO for sinusoidal waveform.
- 25 Determine voltage for resistor connected in series and parallel using a DVM.
- 26 Show that voltage division occurs in a series circuit and voltage is constant in a parallel using a DVM.
- 27 Generate the sinusoidal waveform for different frequency and amplitude using the Function Generator and plot the waveform.
- 28 Generate and plot the waveforms of sinusoidal waves of different frequency and amplitude in the laboratory.
- 29 Measurement of voltage, resistance, current and continuity for a single loop resistive network using DMM.
- 30 Carry out voltage, resistance and current measurement in a single loop resistance network and also check for continuity using DMM.

- 31 Determination of displacement using LVDT transducer
- 32 Carry out linear displacement measurement by using a passive transducer.
- 33 Measure displacement and plot a graph displacement against voltage while using LVDT transducer.
- 34 Measurement of temperature using RTD /thermistor/thermocouple sensors.
- 35 Show how temperature measurement is carried out using RTD/Thermistor /Thermocouple sensors.
- 36 Determination of load/torque/force using strain gauge sensor.

### Allocation of Marks

Sl.No	Description	Marks
1	Aim & Apparatus Required	5
2	Circuit Diagram	20
3	Connections / Execution	25
4	Output / Result	10
5	Written Test	30
6	Viva Voce	10
<b>Total Marks</b>		<b>100</b>